

Assignment 1

Abhishek Thakur
EE20RESCH11014

Download the codes from

https://github.com/abhishekt711/FPGA_Lab/Assignment_1


1 Question:6(a)

Draw the Logic Circuit of the following Boolean Expression:

$$\bar{A}\bar{B} + AC \quad (1)$$

2 Solution

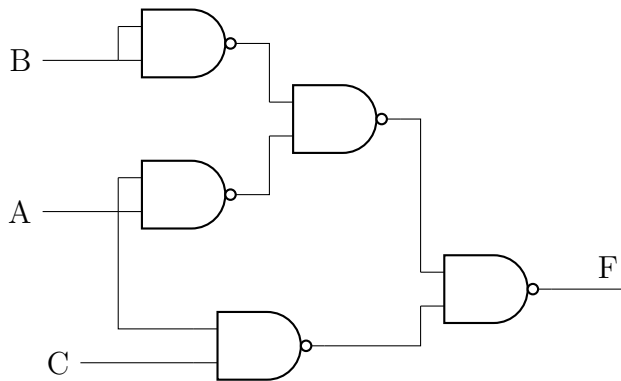The logic circuit for the boolean function $\bar{A}\bar{B} + AC$ can be drawn using only NAND gate as:



$$F = \overline{\overline{\bar{A}\bar{B}AC}} \quad (2)$$

$$F = \overline{\bar{A}\bar{B}} + \overline{AC} \quad (3)$$

$$F = \bar{A}\bar{B} + AC \quad (4)$$